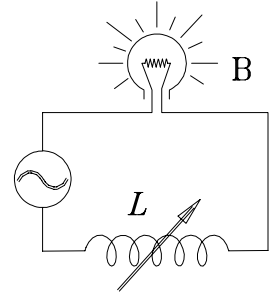


# Physics 108 Assignment # 10 SOLUTIONS: AC CIRCUITS & EM WAVES

Wed. 16 Mar. 2005 — finish by Wed. 23 Mar.



1. **DIMMER SWITCH:** A typical “light dimmer” switch consists of a variable inductor  $L$  connected in series with the light bulb B as shown in the diagram on the right. The power supply produces 120 V (*rms*) at 60.0 Hz and the light bulb is marked “120 V, 100 W.” Assume that the light bulb is a simple resistor whose resistance does not depend on its temperature.

- (a) What maximum inductance  $L$  is required if the power in the light bulb is to be varied by a factor of five?  
**ANSWER:** Since we are looking for a given power *ratio*, the answer will be independent of the rms driving voltage (see below). The frequency is  $\omega = 2\pi(60 \text{ Hz}) = 377 \text{ s}^{-1}$ . The light bulb draws  $P = \mathcal{E}^2/R = 100 \text{ W}$  when the voltage drop across it is  $\mathcal{E} = 120 \text{ V}$ , so  $R = \mathcal{E}^2/P = (120)^2/100 = 144 \Omega$ . Now, for an  $LR$  circuit the impedance is just  $Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + \omega^2 L^2}$  (*i.e.* we just omit the capacitive reactance term)<sup>1</sup> so that  $I_m = \mathcal{E}_m/Z$  and the average power dissipated in the resistance (light bulb) is

$$\bar{P} = \frac{1}{2} I_m^2 R = \frac{R}{2} \cdot \frac{\mathcal{E}_m^2}{Z^2} = \frac{R}{2} \cdot \frac{\mathcal{E}_m^2}{R^2 + \omega^2 L^2}. \text{ When } L \rightarrow 0 \text{ we get a maximum value of } \bar{P}(\text{max}) = \frac{\mathcal{E}_m^2}{2R} \text{ and when}$$


$$L \rightarrow L_{\text{max}} \text{ we get a minimum value of } \bar{P}(\text{min}) = \frac{R}{2} \cdot \frac{\mathcal{E}_m^2}{R^2 + \omega^2 L_{\text{max}}^2}. \text{ We want the ratio of these to be five:}$$

$$\frac{\bar{P}(\text{max})}{\bar{P}(\text{min})} = \frac{R^2 + \omega^2 L_{\text{max}}^2}{R^2} = 5 \implies R^2 + \omega^2 L_{\text{max}}^2 = 5R^2 \implies \omega^2 L_{\text{max}}^2 = 4R^2 \text{ or } \omega L_{\text{max}} = 2R \text{ giving}$$

$$L_{\text{max}} = \frac{2R}{\omega} = \frac{2 \times 144}{377} \text{ or } \boxed{L_{\text{max}} = 0.764 \text{ H}}.$$

- (b) Could one use a variable resistor in place of the variable inductor? If so, what maximum resistance  $R$  would be required? Why isn't this done? (Variable resistors [rheostats] are generally cheaper than variable inductors.)  
**ANSWER:** The circuit would be cheaper to build using a rheostat in place of the variable inductance and it would work fine: the two resistances in series would just add up to one net resistance  $R_{\text{tot}} = R_{\text{light}} + R_{\text{var}}$  so that  $I_{\text{rms}} = \mathcal{E}_{\text{rms}}/R_{\text{tot}}$  and  $\bar{P}_{\text{light}} = I_{\text{rms}}^2 R_{\text{light}} = \mathcal{E}_{\text{rms}}^2 R_{\text{light}} / (R_{\text{light}} + R_{\text{var}})$ , which can be varied from a minimum of  $\mathcal{E}_{\text{rms}}^2 R_{\text{light}} / (R_{\text{light}} + R_{\text{max}})$  to a maximum of  $\mathcal{E}_{\text{rms}}^2 R_{\text{light}}$ , the ratio of which  $[R_{\text{light}} / (R_{\text{light}} + R_{\text{max}})]$  can easily be made equal to 5. The problem with this simpler design is that when the light is *dimmed* ( $\bar{P}_{\text{light}}$  minimized), considerable power  $[I_{\text{rms}}^2 R_{\text{var}}]$  is being uselessly dissipated in the rheostat! A pure inductance, by contrast, does not draw any power; it merely shifts the phase of the voltage and current.

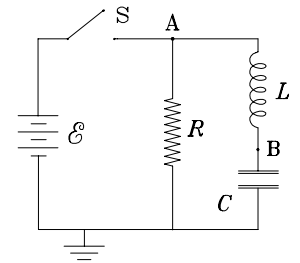2. **LCR CIRCUIT TIME-DEPENDENCE:** In the circuit shown, the battery has negligible internal resistance. The switch **S** is closed for a long time, then opened. Describe *qualitatively* what happens in the circuit after the switch is closed and then after it is opened again, for two cases:



- (a)  $R/2L > 1/\sqrt{LC}$  and  
 (b)  $R/2L < 1/\sqrt{LC}$ .

**ANSWER:** This problem has a tricky part, namely the behaviour when the switch is first closed. In this situation  $\sum \Delta \mathcal{E} = 0$  around the leftmost loop requires that a current  $I_1 = \mathcal{E}/R$  immediately start flowing through  $R$  and continue that way forever. So, for all practical purposes,  $R$  simply serves to drain the battery and has no effect at all on the voltages in the outer loop, which consists of a battery driving an undamped  $LC$  circuit — which will therefore oscillate indefinitely at its resonant frequency  $\omega_0 = 1/\sqrt{LC}$  without any damping at all, regardless of the size of  $R!$

<sup>1</sup>This can be shown rigorously without too much difficulty, but it makes sense that a term due to a nonexistent component should disappear from the formula.

When the switch is opened again, we do get different behaviour depending on the ratio of  $R$  to  $L$ . Specifically, if we define  $\lambda = R/2L$  and  $\omega_0 = 1/\sqrt{LC}$ , for  $\lambda > \omega_0$  we have an “overdamped” oscillator in which the current will decay away exponentially with no oscillations, whereas for  $\lambda < \omega_0$  we will see oscillations at the frequency

$\omega = \sqrt{\omega_0^2 - \lambda^2}$  whose amplitude decays exponentially with a time constant  $\tau = 1/\lambda$ .

3. **ELECTROMAGNETIC WAVE:** The electric field associated with a plane electromagnetic wave is given by

$$E_x = 0, \quad E_y = 0 \quad \text{and} \quad E_z = E_0 \sin[k(x - ct)],$$

where  $E_0 = 2.34 \times 10^{-4}$  V/m and  $k = 9.72 \times 10^6$  m<sup>-1</sup>. The wave is propagating in the  $+x$  direction.

- (a) Write expressions for all three components of the magnetic field associated with the wave.

**ANSWER:** The wave propagates in the direction given by  $\vec{E} \times \vec{B}$  (see textbook’s section on the POYNTING VECTOR) and so, since  $\vec{E}$  points in the  $\hat{k}$  direction and the wave propagates in the  $\hat{i}$  direction, we must have  $\hat{i} = \hat{k} \times \hat{B}$  where  $\hat{B}$  is the unit vector in the  $\vec{B}$  direction. The only unit vector satisfying this criterion is  $\hat{B} = -\hat{j}$  and so  $\vec{B}$  is in the negative  $y$  direction when  $\vec{E}$  is in the positive  $z$  direction. Both must oscillate sinusoidally with the same wavelength and frequency, so they share the same propagation speed  $c$ , the same wavenumber  $k$  and the same angular frequency  $\omega = ck$ . This allows us to write down the answer:

$$B_x = B_z = 0 \quad \text{and} \quad B_y = -B_0 \sin[k(x - ct)].$$

Having established this, we need only find the relationship between the amplitudes of the  $E$  and  $B$  fields. Their magnitudes must satisfy  $|\frac{\partial E}{\partial x}| = |\frac{\partial B}{\partial t}|$ , giving  $kE_0 = \omega B_0$  or  $B_0 = \frac{k}{\omega} E_0$  or

$$B_0 = E_0/c = \frac{2.34 \times 10^{-4}}{2.997 \times 10^8} = 0.7805 \times 10^{-12} \text{ T}. \quad (\text{This also follows from } E = cB \text{ [always valid].})$$

- (b) Find the wavelength of the wave. **ANSWER:** All you need for this part is the universal relationship

$$k \equiv \frac{2\pi}{\lambda} \implies \lambda = \frac{2\pi}{k} = \frac{2\pi}{9.72 \times 10^6}$$

or  $\lambda = 0.6464 \times 10^{-6} \text{ m} = 0.6464 \mu\text{m}$ .

NOTE: This was a rather trivial problem, designed partly to remind you of the properties of waves, our subject for most of the rest of the course. I have been rather longwinded in the solutions; you may be much more economical with words, but be sure you always make your basic reasoning clear!