

AC RC CIRCUITS

A useful introduction to **AC circuits** can be developed using only **resistance** R and **capacitance** C . Picture an RC circuit driven by a sinusoidal voltage


$$\mathcal{E}(t) = \mathcal{E}_0 \cos(\omega t) = \Re e^{i\omega t}$$

where \Re signifies “the real part of” a complex quantity like $e^{i\theta} = \cos \theta + i \sin \theta$. The imaginary part is written (e.g.) $\Im e^{i\theta} = \sin \theta$.

(Physical quantities like current or voltage don’t actually have a measurable imaginary part, of course.)

The voltage *amplitude* \mathcal{E}_0 is taken to be pure real.

An RC circuit driven by an AC voltage:

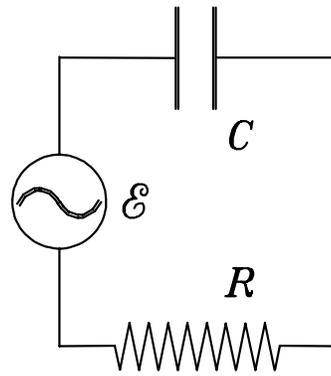

Kirchhoff's rule $\sum_i \Delta V_i = 0$ gives

$$\mathcal{E} - \frac{Q}{C} - R \frac{dQ}{dt} = 0 . \quad (1)$$

The only plausible “steady-state” motion is for Q to oscillate at the same frequency as the driving voltage. We express this expectation as a **trial solution**:

$$Q(t) = Q_0 e^{i\omega t} . \quad (2)$$

Let's see if this trial solution (2) "works" [satisfies the differential equation]. The complex exponential form is easy to differentiate: each time derivative of $Q(t)$ just "pulls down" another factor of $i\omega$. Thus

$$\mathcal{E}_0 e^{i\omega t} - \frac{1}{C} Q_0 e^{i\omega t} - i\omega R Q_0 e^{i\omega t} = 0, \quad (3)$$

from which we can remove the common factor $e^{i\omega t}$ and do a little algebra to obtain

$$Q_0 = \frac{\mathcal{E}_0/R}{1/RC + i\omega} = \frac{\mathcal{E}_0/R}{\lambda + i\omega} \quad (4)$$

where

$$\lambda \equiv \frac{1}{RC} \equiv \frac{1}{\tau}. \quad (5)$$

Now, the charge on a capacitor can't be measured directly. What we want to know is the *current* $I \equiv \dot{Q}$. Since the entire time dependence of Q is in the factor $e^{i\omega t}$, we have trivially

$$I(t) = i\omega Q(t) = I_0 e^{i\omega t} \quad (6)$$

where

$$I_0 = i\omega Q_0 = \frac{i\omega \mathcal{E}_0 / R}{\lambda + i\omega} = \frac{\mathcal{E}_0 / R}{1 - i\lambda / \omega} = \frac{\mathcal{E}_0}{R - i / \omega C}. \quad (7)$$

Since \mathcal{E} , Q and I all have the same time dependence except for differences of *phase* encoded in the complex amplitudes Q_0 and I_0 , we can think in terms of an *effective resistance* R_{eff} such that

$$\mathcal{E} = I R_{\text{eff}} \quad \text{or} \quad R_{\text{eff}} = \frac{\mathcal{E}_0}{I_0}. \quad (8)$$

With a little more algebra we can write the effective resistance in the form

$$R_{\text{eff}} = R - iX_C \quad (9)$$

where


$$X_C \equiv \frac{1}{\omega C} \quad (10)$$

is the *capacitive reactance* of the circuit. This is a quantity that “acts like” (and has the units of) a *resistance* — just like R , the first term in R_{eff} .

The *current* through the circuit cannot be different in different places (due to charge conservation) and follows the time dependence of the driving voltage but (because R_{eff} is generally complex) is not generally *in phase* with it, nor with the *voltage drop* across C :

$$\begin{aligned} -\Delta\mathcal{E}_R &= IR, & \text{but} \\ -\Delta\mathcal{E}_C &= -iIX_C. \end{aligned} \tag{11}$$

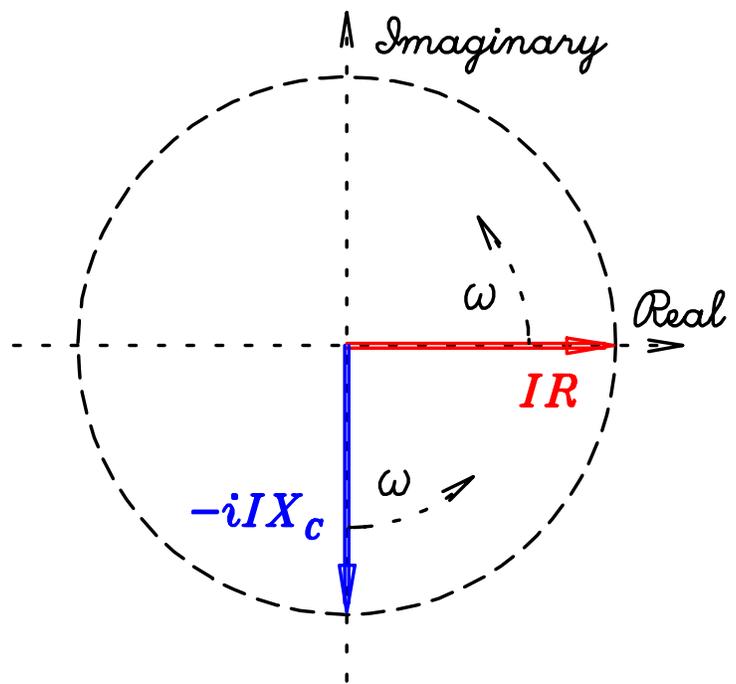The **Phase Circle** shows the voltage drops in “complex phase space” as **vectors** that *rotate* at a constant frequency ω .



The voltage across the *capacitor lags behind* that across the resistor by an angle of $\pi/2$.

At any instant the actual, *measurable* value of any voltage is just its *real* part — *i.e.* the projection of its complex vector onto the real axis.

Power

From the point of view of the power supply,* the circuit is a “black box” that “resists” the applied voltage with a weird “back \mathcal{EMF} ” ($\mathcal{E}_{\text{back}}$) given by R_{eff} times the current I — *i.e.* by the sum of both terms in Eq. (11) or the sum of the two vectors in the *Phase Circle*.

*Please forgive my anthropomorphization of circuit elements; these metaphors help me remember their “behaviour”.

The *power* dissipated in the circuit is the product of the real part of the applied voltage[†] and the real part of the resultant current[‡]

$$\begin{aligned} P(t) &= \Re \mathcal{E} \times \Re I = \Re (\mathcal{E}_0 e^{i\omega t}) \Re (I_0 e^{i\omega t}) \\ &= \mathcal{E}_0^2 \Re \left(\frac{1}{R_{\text{eff}}} \right) \cos^2(\omega t) . \end{aligned} \quad (12)$$

which oscillates at a frequency 2ω between zero and its maximum value

$$P_{\text{max}} = \mathcal{E}_0^2 \Re \left(\frac{1}{R_{\text{eff}}} \right) \quad (13)$$

[†]The imaginary voltage component doesn't generate any power.

[‡]Neither does the imaginary part of the current.

so that the *average* power drain is[§]

$$\langle P \rangle = \frac{1}{2} \varepsilon_0^2 \left[\frac{R}{R^2 + X_C^2} \right] = \varepsilon_{\text{rms}} I_{\text{rms}} \cos \phi \quad (14)$$

where $\varepsilon_{\text{rms}} = \varepsilon_0 / \sqrt{2}$, I_{rms} is the root-mean-square current in the circuit,

$$\cos \phi = \frac{R}{Z} \quad (15)$$

is the “*power factor*” of the *RC* circuit and

$$Z \equiv \sqrt{R^2 + X_C^2} \quad (16)$$

is the *impedance* of the circuit.

[§]I have used $\frac{1}{x + iy} = \frac{x - iy}{x^2 + y^2}$ to obtain the real part of $1/R_{\text{eff}}$.

Expressing the average power dissipation in this form allows one to think of an **AC RC** circuit the same way as a DC **RC** circuit with the *power factor* as a sort of “fudge factor” .

This all gets a lot more interesting when we add the “inertial” effects of an **inductance** to our circuit. Stay tuned.